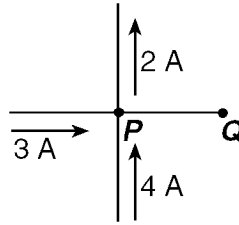


Name: _____





Power, Energy and Kirchoff's Rules Worksheet

- 1) The diagram below shows electric currents in conductors that meet at junction P .







What are the magnitude and direction of the current in conductor PQ ?

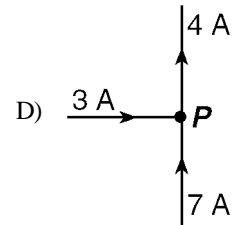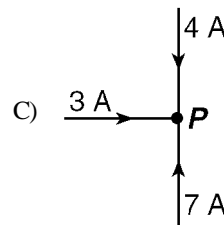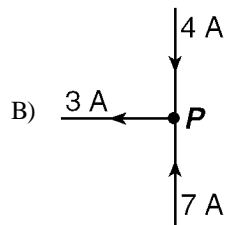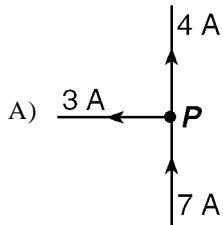
- A) 9 A toward P B) 9 A toward Q C) 5 A toward Q D) 5 A toward P
- 2) Which diagram below correctly shows currents traveling near junction P in an electric circuit?



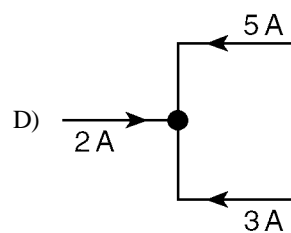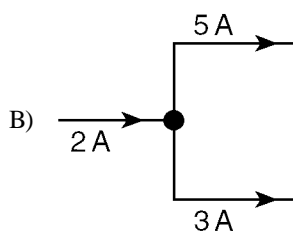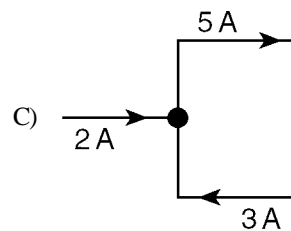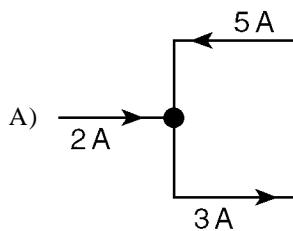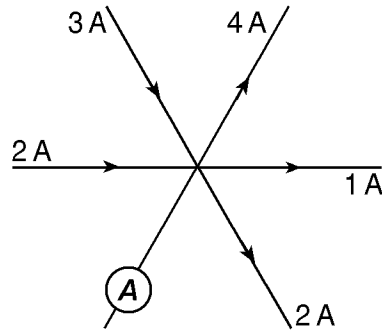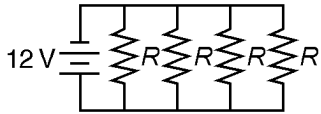

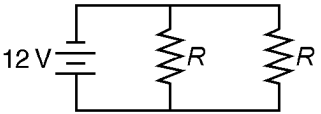
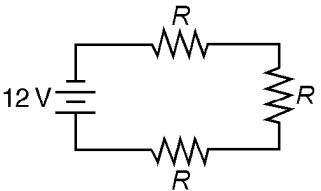
- 3) Which diagram shows correct current direction in a segment of an electric circuit?



- 4) The diagram below represents currents in a segment of an electric circuit.



What is the reading of ammeter A ?

- A) 1 A B) 2 A C) 3 A D) 4 A
- 5) Identical resistors (R) are connected across the same 12-volt battery. Which circuit uses the *greatest* power?
- A) 
- B) 
- C) 
- D) 
- 6) A potential drop of 50. volts is measured across a 250-ohm resistor. What is the power developed in the resistor?
- 7) In a series circuit containing two lamps, the battery supplies a potential difference of 1.5 volts. If the current in the circuit is 0.10 ampere, at what rate does the circuit use energy?
- A) 15 W B) 1.5 W C) 0.15 W D) 0.015 W
- 8) While operating at 120 volts, an electric toaster has a resistance of 15 ohms. What is the power used by the toaster?
- 9) A microwave oven operating at 120 volts is used to heat a hot dog. If the oven draws 12.5 amperes of current for 45 seconds, what is the power dissipated by the oven?
- 10) What is the total electrical energy used by a 1,500-watt hair dryer operating for 6.0 minutes?
- 11) An operating electric heater draws a current of 10. amperes and has a resistance of 12 ohms. How much energy does the heater use in 60. seconds?