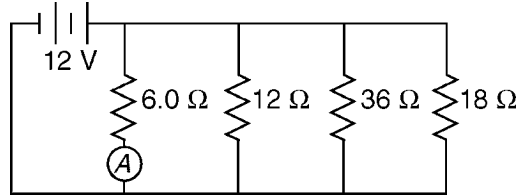


Name: _____





Series and Parallel Circuits Worksheet

Questions 1 and 2 refer to the following:

The diagram below represents an electric circuit consisting of four resistors and a 12-volt battery.




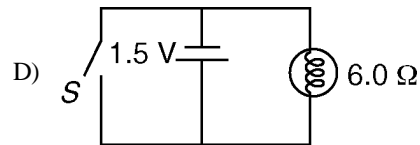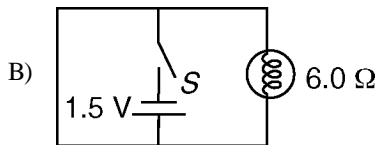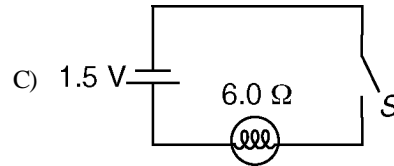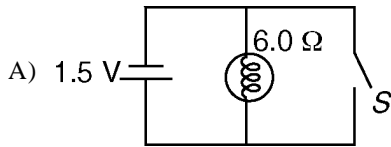- 1) What is the current measured by ammeter A shown in the diagram?
- 2) What is the equivalent resistance of the circuit shown?
- 3) A 6.0-ohm lamp requires 0.25 ampere of current to operate. In which circuit below would the lamp operate correctly when switch S is closed?



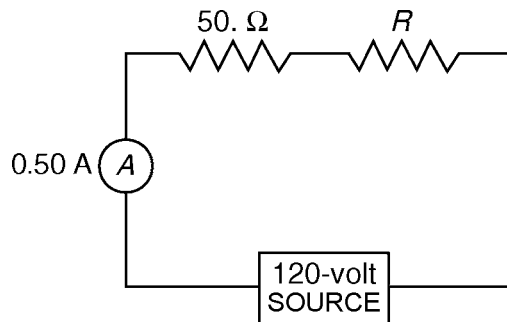Questions 4 and 5 refer to the following:


A 50.-ohm resistor, an unknown resistor R , a 120-volt source, and an ammeter are connected in a complete circuit. The ammeter reads 0.50 ampere.



- 4) Calculate the equivalent resistance of the circuit shown. [Show all work, including the equation and substitution with units.]
- 5) Determine the resistance of resistor R shown in the diagram.

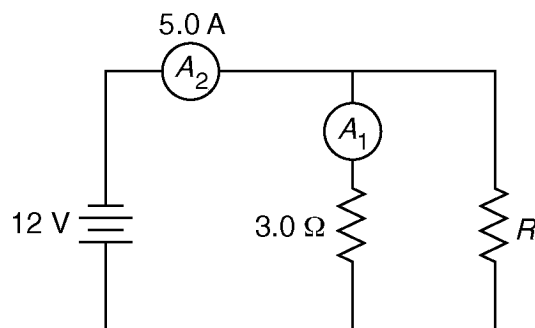Questions 6 through 8 refer to the following:

A 3.0-ohm resistor, an unknown resistor, R , and two ammeters, A_1 and A_2 , are connected as shown below with a 12-volt source. Ammeter A_2 reads a current of 5.0 amperes.



- 6) Determine the equivalent resistance of the circuit shown.
- 7) Calculate the current measured by ammeter A_1 in the diagram shown. [Show all work, including the equation and substitution with units.]
- 8) Calculate the resistance of the unknown resistor, R in the diagram shown. [Show all work, including the equation and substitution with units.]